

ELEC1323 Communications

4 Coherent detection

Non-coherent vs coherent detection (CEP 3.6)

- In an AM signal, the sidebands contain all of the message information. The carrier contains none.
- However, in order to avoid overmodulation and allow **non-coherent** envelope detection, the carrier must use at least $2/3$ of the transmit power.
- If we want a more power-efficient AM scheme, we need to overmodulate the carrier and use **coherent** detection.
- However, this requires a more complicated receiver, which can obtain exact knowledge of the carrier **frequency** and **phase**.

Coherent detection (CEP 3.5.2)

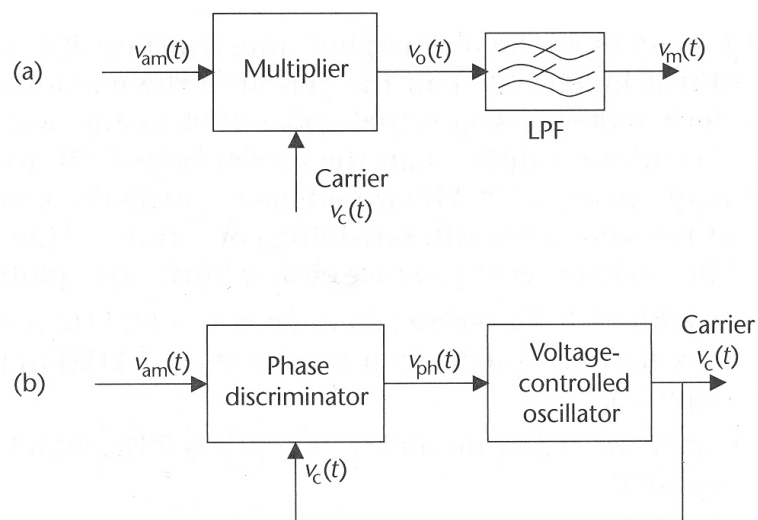


Figure 3.20 (a) Coherent AM demodulator; (b) phase-locked loop (PLL).

- The **VCO** produces a sinusoid $v_c(t)$ having the frequency f_c when its input $v_{ph}(t)$ is zero.
- This frequency is increased or decreased when the input is positive or negative, respectively.
- The output of the **phase discriminator** $v_{ph}(t)$ will be zero when $v_c(t)$ and $v_{am}(t)$ are in phase, otherwise it will be positive or negative as appropriate.
- The negative feedback loop keeps $v_c(t)$ and $v_{am}(t)$ in phase.

Coherent detection (CEP 3.5.2)


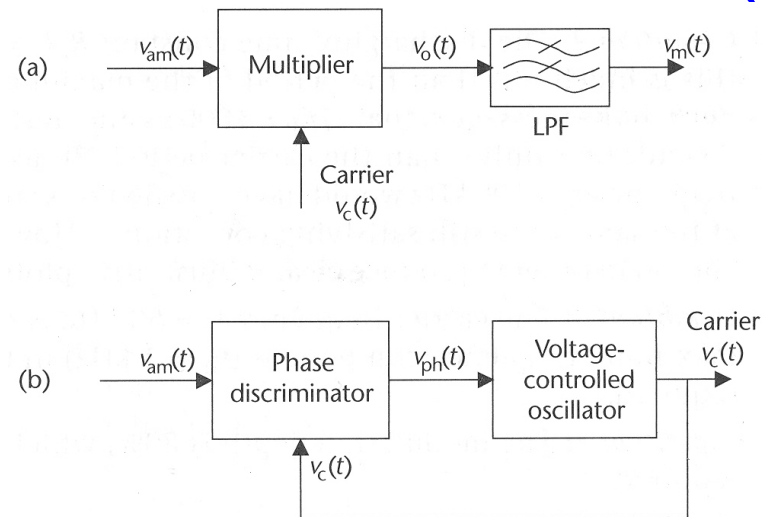


Figure 3.20 (a) Coherent AM demodulator; (b) phase-locked loop (PLL).
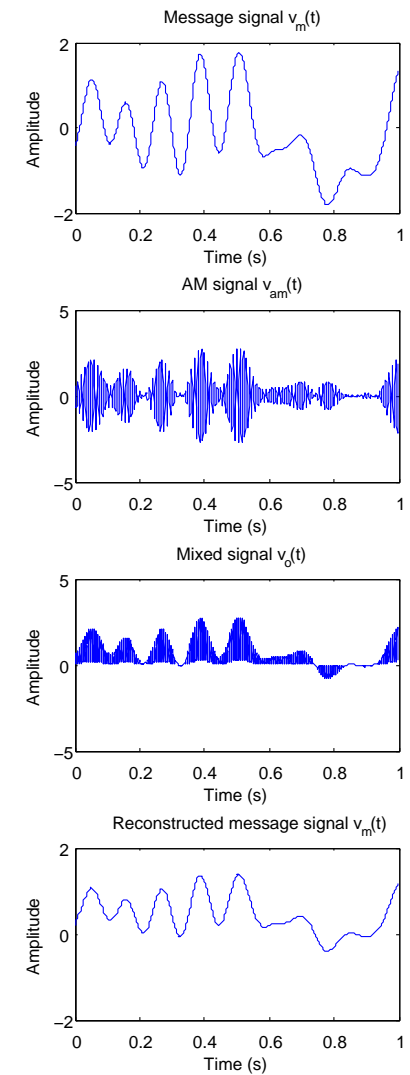
$$\begin{aligned}
 v_{am}(t) &= (V_c + k_{am} \cdot v_m(t)) \cos(2\pi f_c t) \\
 v_c(t) &= \cos(2\pi f_c t) \\
 v_o(t) &= v_{am}(t) \cdot v_c(t) \\
 &= (V_c + k_{am} \cdot v_m(t)) \cos^2(2\pi f_c t)
 \end{aligned}$$



Coherent detection (CEP 3.5.2)


$$v_o(t) = (V_c + k_{am} \cdot v_m(t)) \cos^2(2\pi f_c t)$$

Using the trigonometric identity $\cos^2(2\pi f t) = \frac{1}{2} + \frac{1}{2} \cos(4\pi f t)$ from lecture 3, we get

$$\begin{aligned} v_o(t) &= (V_c + k_{am} \cdot v_m(t)) \left(\frac{1}{2} + \frac{1}{2} \cos(4\pi f_c t) \right) \\ &= \frac{1}{2}(V_c + k_{am} \cdot v_m(t)) + \frac{1}{2}(V_c + k_{am} \cdot v_m(t)) \cos(4\pi f_c t) \end{aligned}$$

The LPF removes the high frequency component, leaving
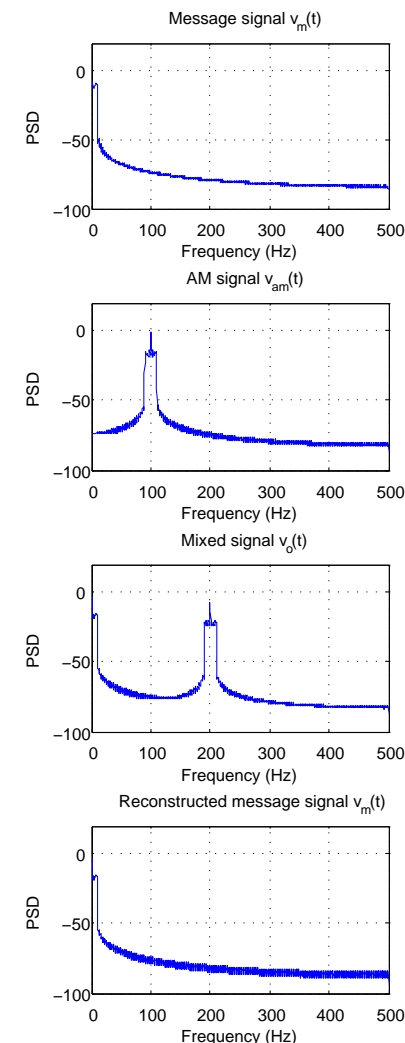
$$v'_m(t) = \frac{1}{2}(V_c + k_{am} \cdot v_m(t))$$



Double SideBand Suppressed Carrier modulation (CEP 3.7.1.1)

DSBSC modulation is like AM modulation, but without the **DC offset**.


$$v_{dsb}(t) = v_m(t) \cdot V_c \cos(2\pi f_c t)$$

For a sinusoidal signal $v_m(t) = V_m \cos(2\pi f_m t)$ we have

$$\begin{aligned} v_{dsb}(t) &= V_m \cos(2\pi f_m t) \cdot V_c \cos(2\pi f_c t) \\ &= \frac{1}{2} V_m V_c \cos(2\pi [f_c - f_m] t) \\ &+ \frac{1}{2} V_m V_c \cos(2\pi [f_c + f_m] t) \end{aligned}$$


The lower and upper side frequencies are retained, but the carrier is suppressed, improving the **power efficiency**. However, the DSBSC signal bandwidth is still double that of the message signal.

Figure 3.29

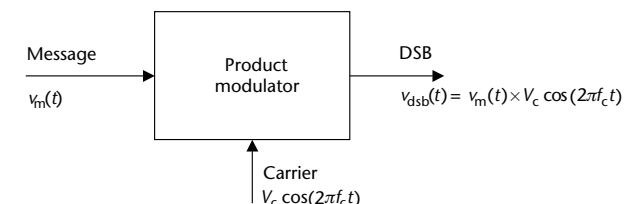

Taken from *Communication Engineering Principles*, © Ifiok Otung, published 2001 by Palgrave

Figure 3.24

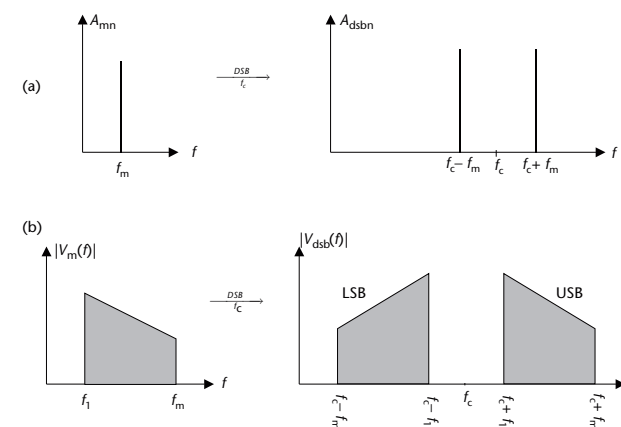


Taken from *Communication Engineering Principles*, © Ifiok Otung, published 2001 by Palgrave

Double SideBand Suppressed Carrier modulation (CEP 3.7.1.1)

In the time domain, the envelope crosses the x axis, causing phase reversals.


Figure 3.23

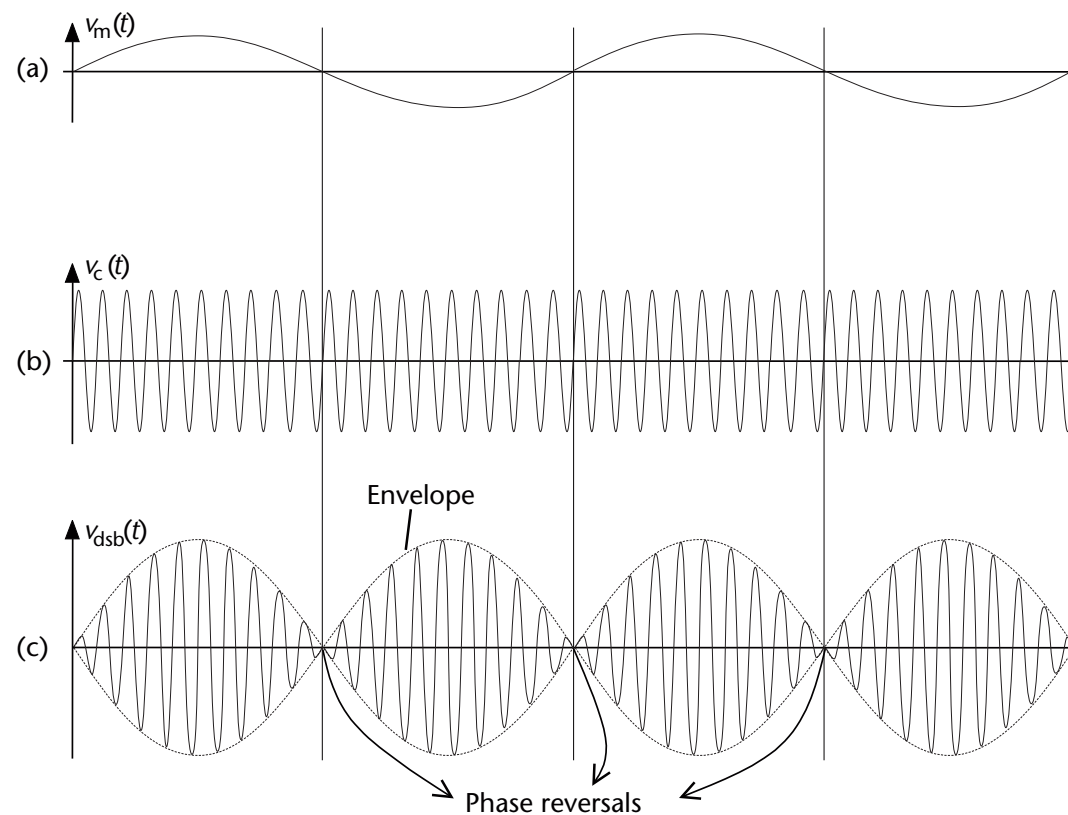

Taken from *Communication Engineering Principles*, © Ifiok Otung, published 2001 by Palgrave

DSBSC modulator (CEP 3.7.1.2)


Figure 3.25

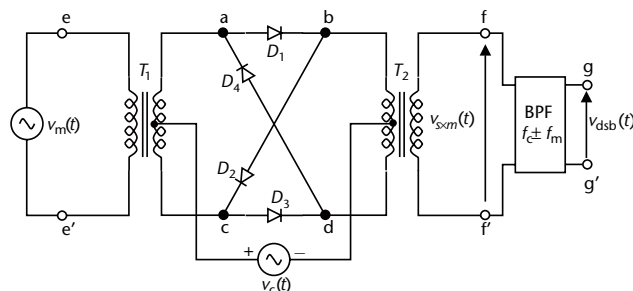

Taken from *Communication Engineering Principles*, © Ifiok Otung, published 2001 by Palgrave


- In a **balanced modulator**, a positive- and negative-going square wave $v_c(t)$ having the carrier frequency f_c is used to bias the **diodes**.
- When the square wave has a positive voltage, D1 and D3 turn on, giving circuit (a). When the voltage is negative, D2 and D4 turn on, giving circuit (b).
- The **BPF** turns the enveloped square wave into an enveloped sinusoid.

Figure 3.27

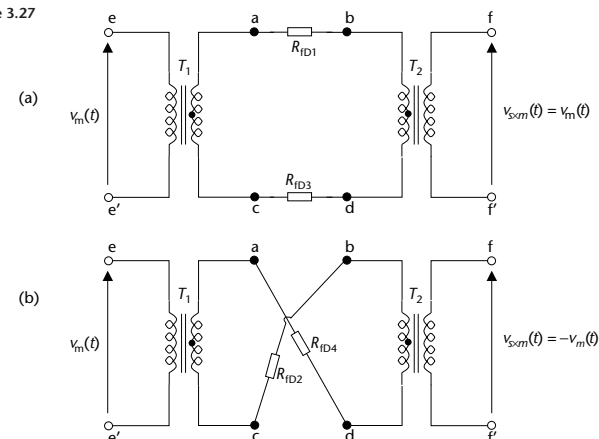

Taken from *Communication Engineering Principles*, © Ifiok Otung, published 2001 by Palgrave

Figure 3.28

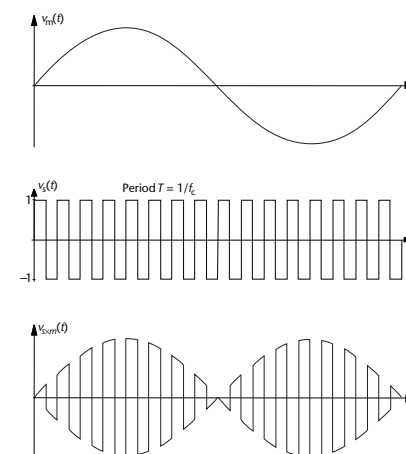

Taken from *Communication Engineering Principles*, © Ifiok Otung, published 2001 by Palgrave

DSBSC demodulator (CEP 3.7.1.3)

Since the DSBSC signal is overmodulated, we must use **coherent demodulation**.

$$v_o(t) = v_{dsb}(t) \cdot v_{LO}(t)$$

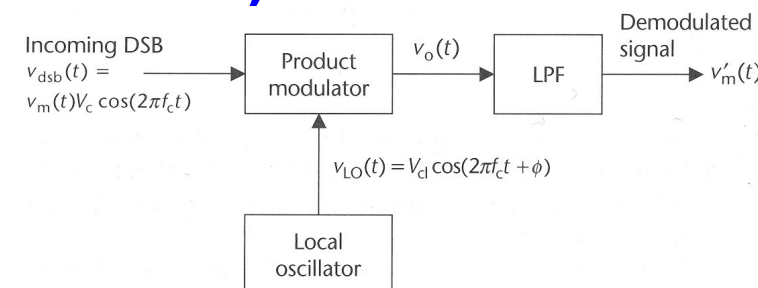


Figure 3.30 Coherent demodulation of DSB.

We can use trigonometric identity (1) from lecture 3 to see what happens when there is a **phase difference** ϕ between the local oscillator and the carrier.

$$\begin{aligned} v_o(t) &= v_m(t)V_c \cos(2\pi f_c t) \cdot V_{cl} \cos(2\pi f_c t + \phi) \\ &= \frac{1}{2}v_m(t)V_c V_{cl} \cos(\phi) + \frac{1}{2}v_m(t)V_c V_{cl} \cos(4\pi f_c t + \phi) \end{aligned}$$

After the LPF we get


$$v'_m(t) = \frac{1}{2}v_m(t)V_c V_{cl} \cos(\phi)$$

Note that $v'_m(t)$ is attenuated altogether when $\phi = \pi/2$, which corresponds to a 90° phase difference. This is the **quadrature null effect**.

DSBSC demodulator (CEP 3.7.1.3)

The quadrature null effect motivates the Costas loop.

Figure 3.31

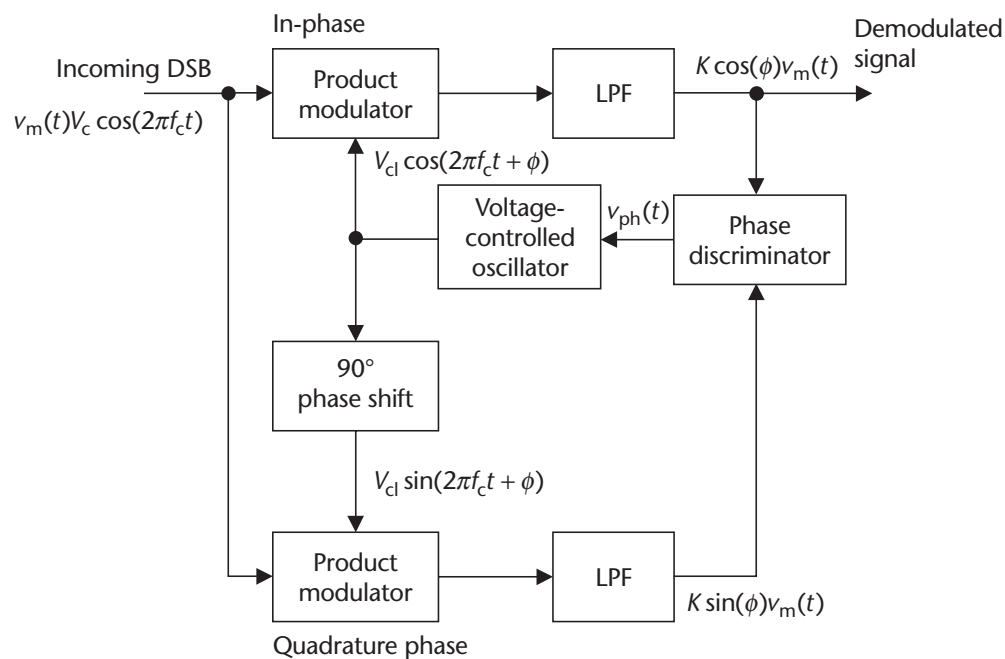

Taken from *Communication Engineering Principles*, © Ifiok Otung, published 2001 by Palgrave

This adjusts the local oscillator frequency until the signal $K \sin(\phi)v_m(t)$ is completely attenuated, leaving the desired signal $K \cos(\phi)v_m(t)$ completely unattenuated.

Tuned receiver (CEP 3.5.3 and 3.5.3.1)

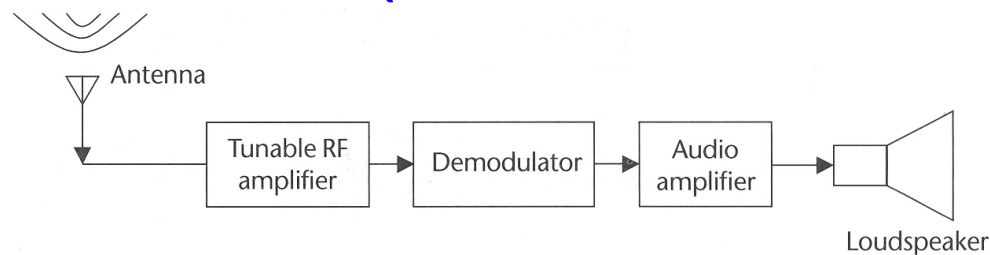


Figure 3.21 Tunable radio frequency (TRF) receiver.

- The **tunable RF amplifier** rejects all signals except for the desired one.
- However, a very complex design is required to achieve the **high-selectivity** necessary to reject the unwanted adjacent signals owing to their **high frequencies**.

Superheterodyne receiver (CEP 3.5.3.2)


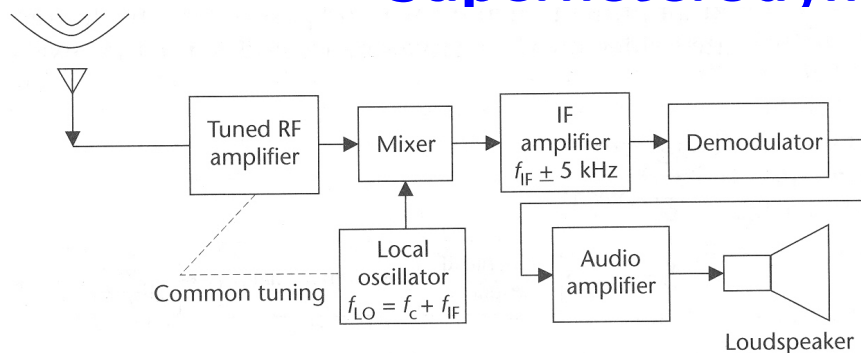


Figure 3.22 The superheterodyne AM receiver.

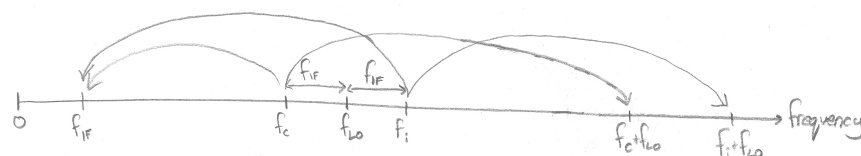

- The **mixer** multiplies the AM signal by a sinusoid having a frequency $f_{LO} = f_c + f_{IF}$, where $f_{IF} \ll f_c$.
- The **mixer** moves the AM signal from being centred at f_c to the difference $f_{LO} - f_c = f_{IF}$ and sum $f_{LO} + f_c = 2f_c + f_{IF}$ of the frequencies f_{LO} and f_c .
- The **high-selectivity IF amplifier** removes the unwanted signals at **low frequencies** adjacent to f_{IF} , as well as the high frequency replica centred at the sum frequency $2f_c + f_{IF}$.
- However, the **mixer** will also move an unwanted image signal centred at $f_i = f_{LO} + f_{IF} = f_c + 2f_{IF}$ to f_{IF} . The **low-selectivity tuned RF amplifier** is therefore required to remove the **high-frequency** image signal before mixing takes place.
- A low complexity design results because **high-selectivity** is only used at **low frequencies**. At **high frequencies**, **low-selectivity** is used.

Exercise

1. Sketch the amplitude spectrum of the message signal $v_m(t) = 3 \cos(20\pi t + \pi/4) + 2 \sin(60\pi t) - \cos(100\pi t)$.
2. Sketch the amplitude spectrum of the signal $v_{am}(t)$ that results when $v_m(t)$ is AM modulated onto a 1 kHz carrier using a DC offset of $V_c = 1$ and a modulation sensitivity of $k_{am} = 0.5$.
3. Calculate the fraction of the transmit power that is in the sidebands.
4. What kind of demodulation is required to recover the message signal $v_m(t)$ and why? Sketch the amplitude spectrum of the signal $v_o(t)$ obtained after the first step of the demodulator.
5. Sketch the phase spectra of the signals $v_m(t)$, $v_{am}(t)$ and $v_o(t)$.